## **ALU Circuit Design Project**

Jawza Fahad Alanazi


443020299


CS125

371

Task 1:


## FA-1BIT

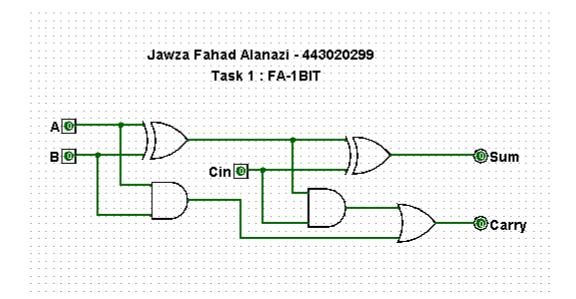


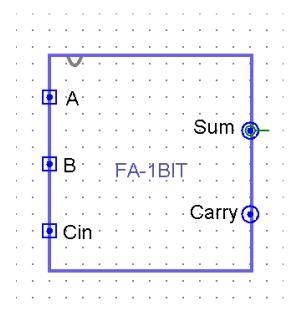

Task 2:

## ALU-1BIT

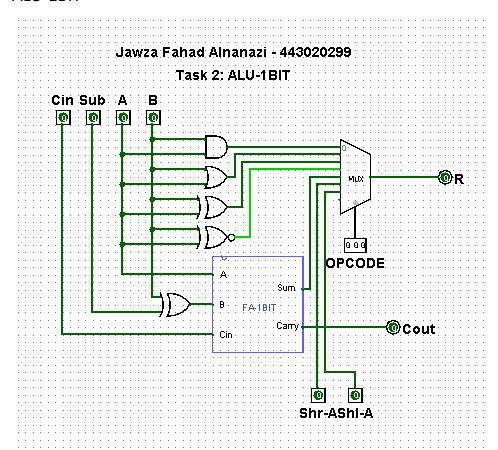

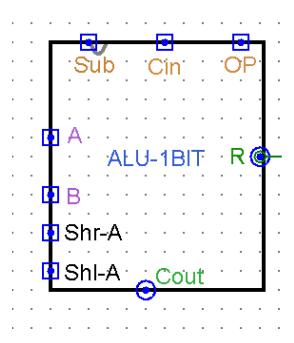

Task 3 & 4:
ALU & Shift Operations

